
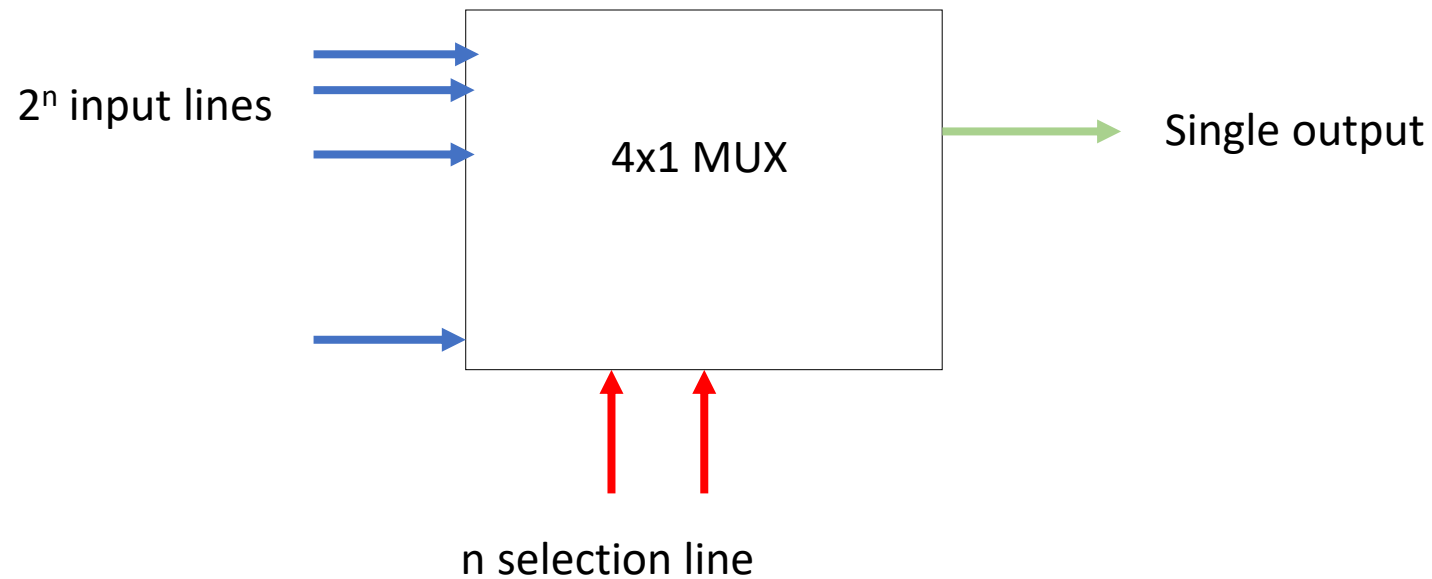


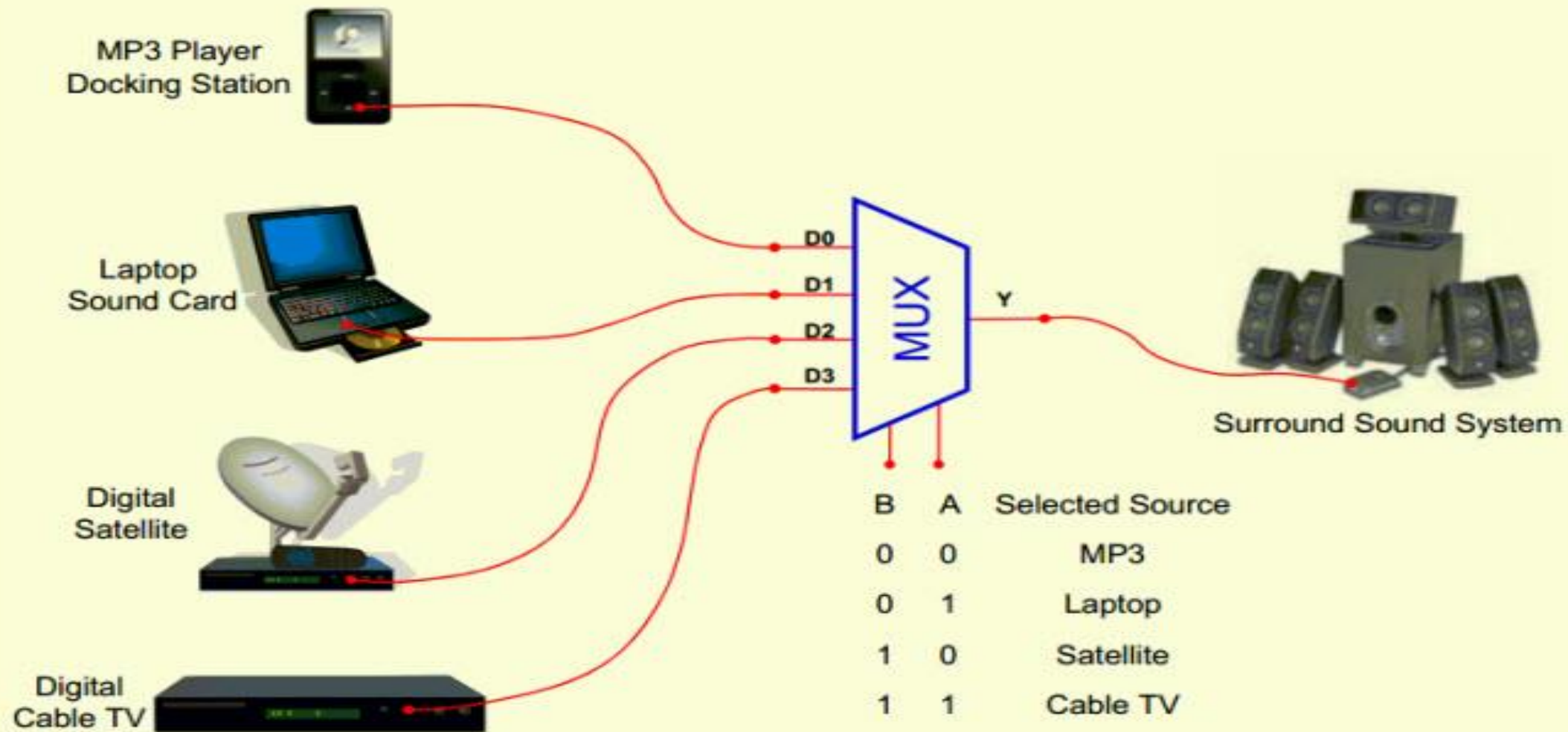
# Multiplexer(Data selector):

- The term multiplex means 'many to one' . Multiplexing is the process of transmitting many number of information in a single line.
- It is also called a data selector since it selects one of many inputs and steers the information to the output.






# 2x1 multiplexer:

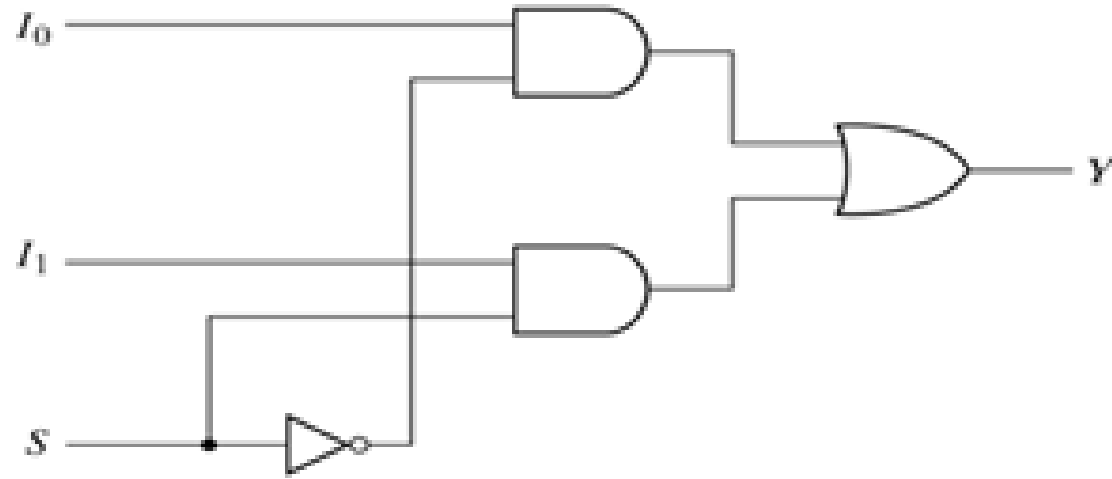

(a) Logic diagram

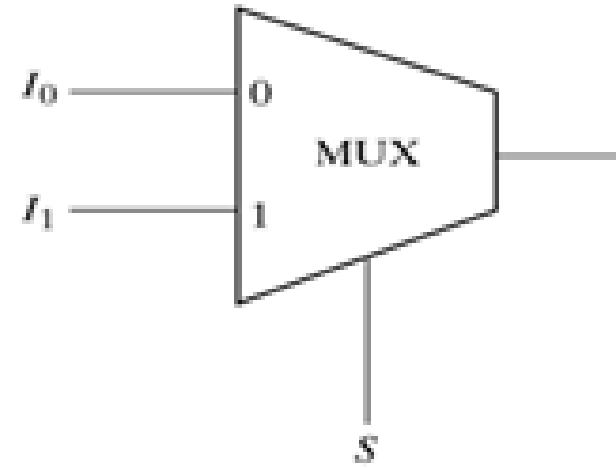


(b) Block diagram

| S | Y     |
|---|-------|
| 0 | $I_0$ |
| 1 | $I_1$ |

$$Y = S'I_0 + S I_1$$
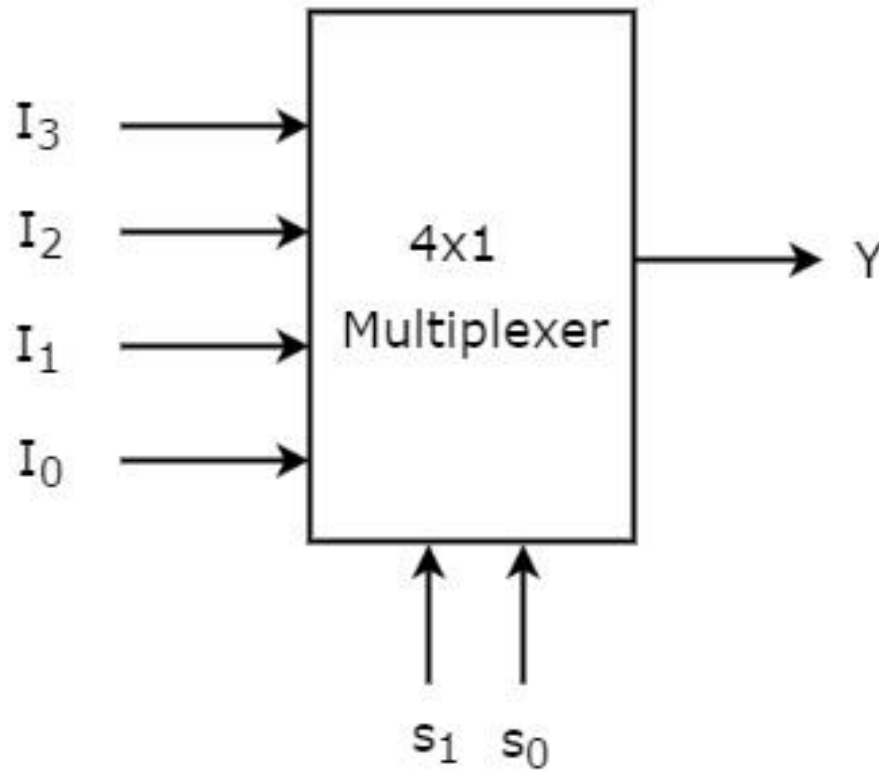
# 4x1 Multiplexer

- 4x1 Multiplexer has four data inputs  $I_3$ ,  $I_2$ ,  $I_1$  &  $I_0$ , two selection lines  $s_1$  &  $s_0$  and one output  $Y$ .




| Selection Lines |       | Output |
|-----------------|-------|--------|
| $S_1$           | $S_0$ | $Y$    |
| 0               | 0     | $I_0$  |
| 0               | 1     | $I_1$  |
| 1               | 0     | $I_2$  |
| 1               | 1     | $I_3$  |

$$Y = S_1'S_0'I_0 + S_1'S_0I_1 + S_1S_0'I_2 + S_1S_0I_3$$
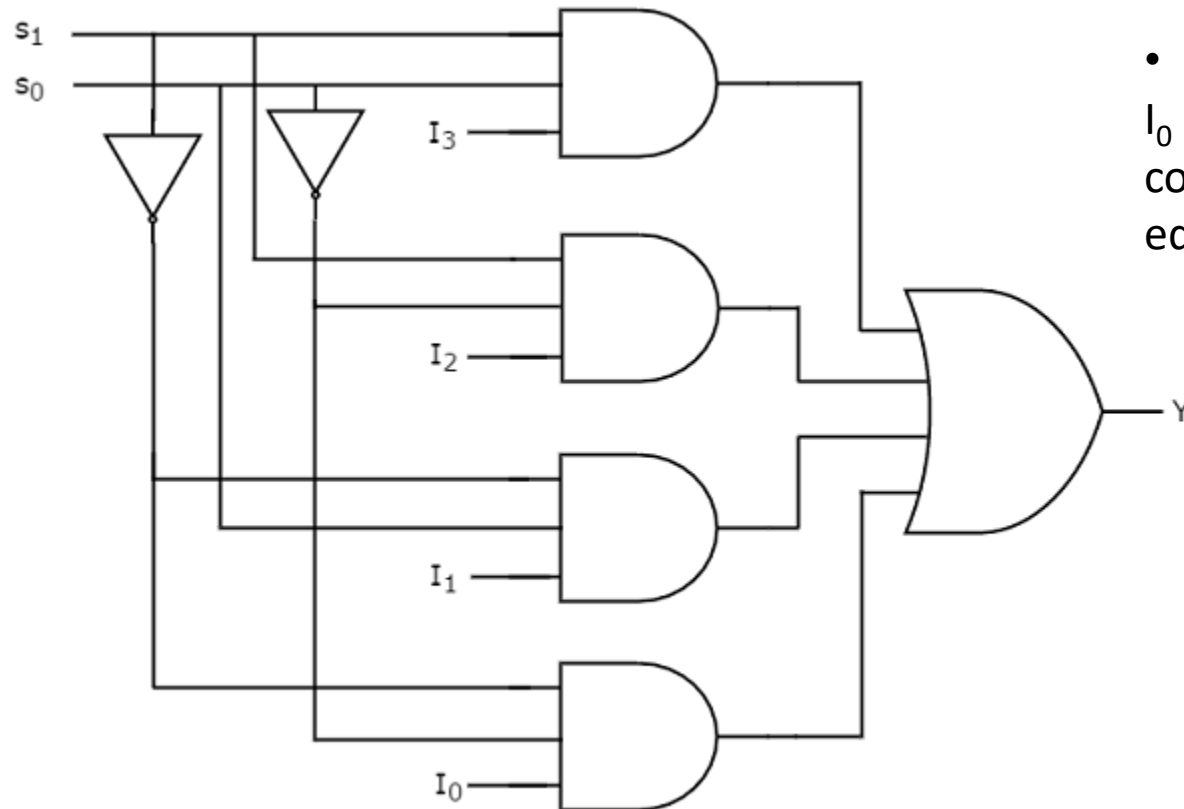
# 4x1 Multiplexer logic diagram


$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$



- When  $S_0 S_1 = 00$  AND gate associated with data input  $I_0$  has two of its input is equal to 1 and third input is connected  $I_0$ . other three AND gates at least one input equal to zero.


# Boolean function implementation Using MUX

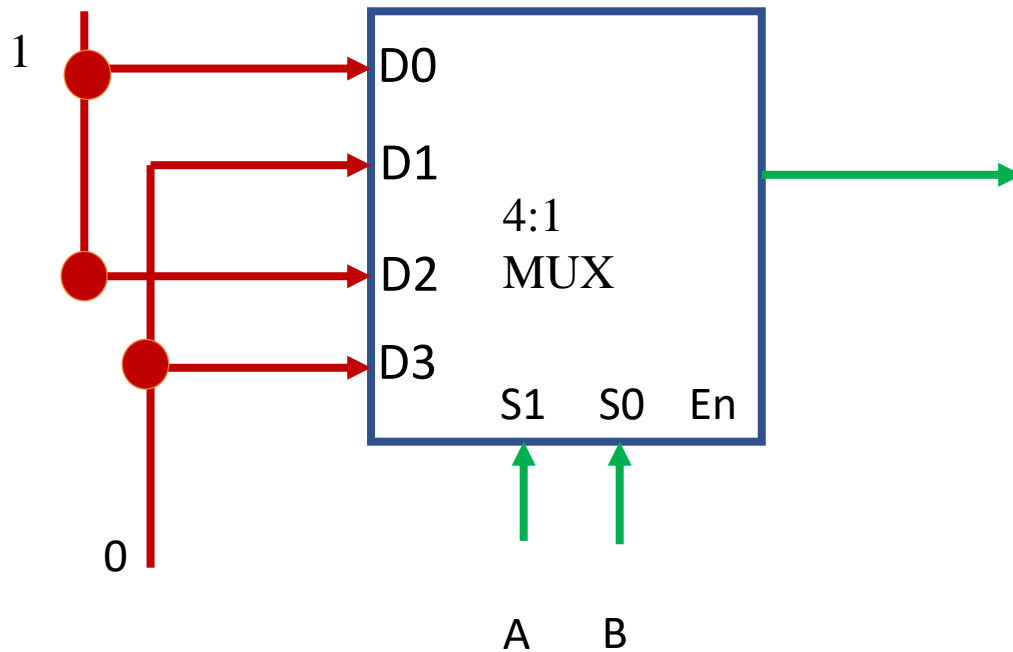1. Implement the following Boolean function using 4:1 mux  $f(A,B) = \sum(0,2)$




Connect the minterms (D0,D2) to high and other (D1,D3) to low.

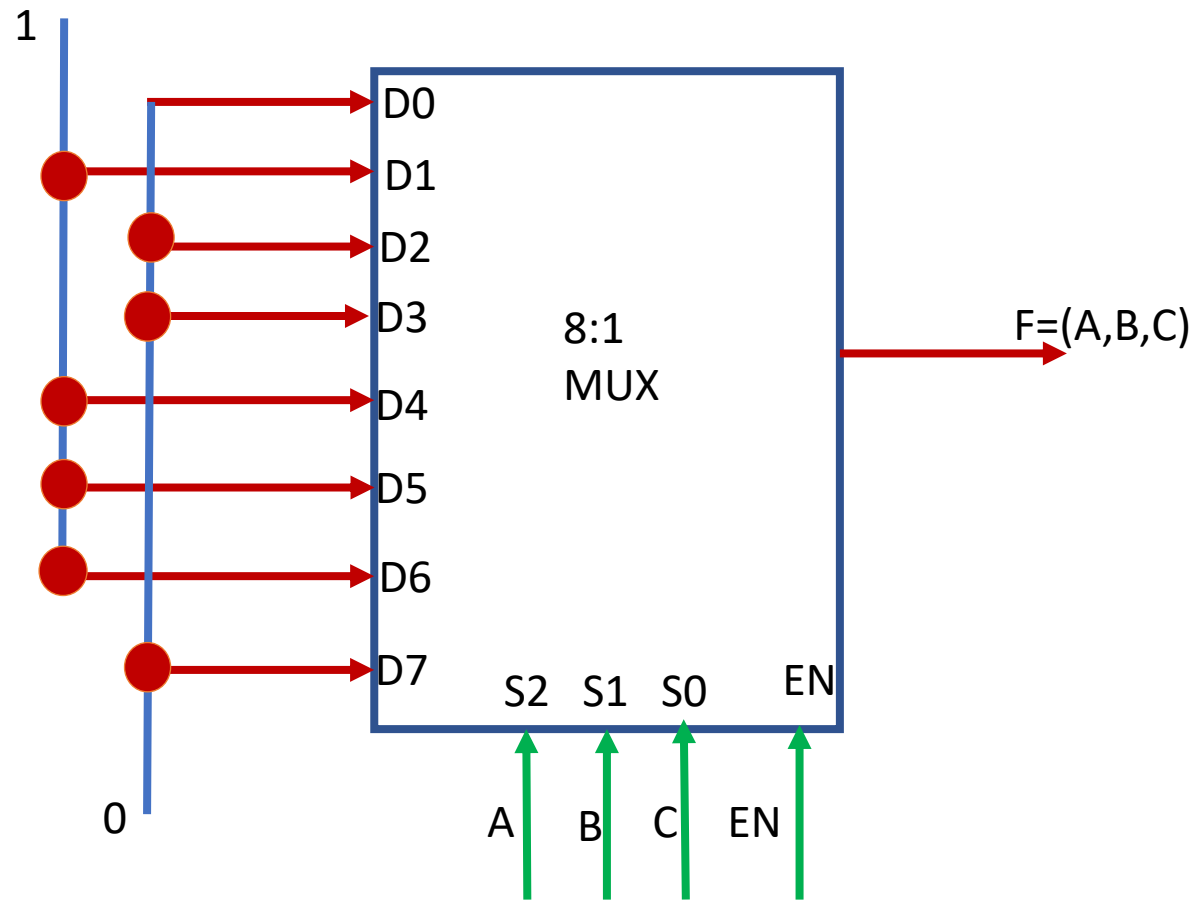- Implement the following Boolean function using 8:1 multiplexer.  
 $F(A,B,C) = \sum(1,4,5,6)$



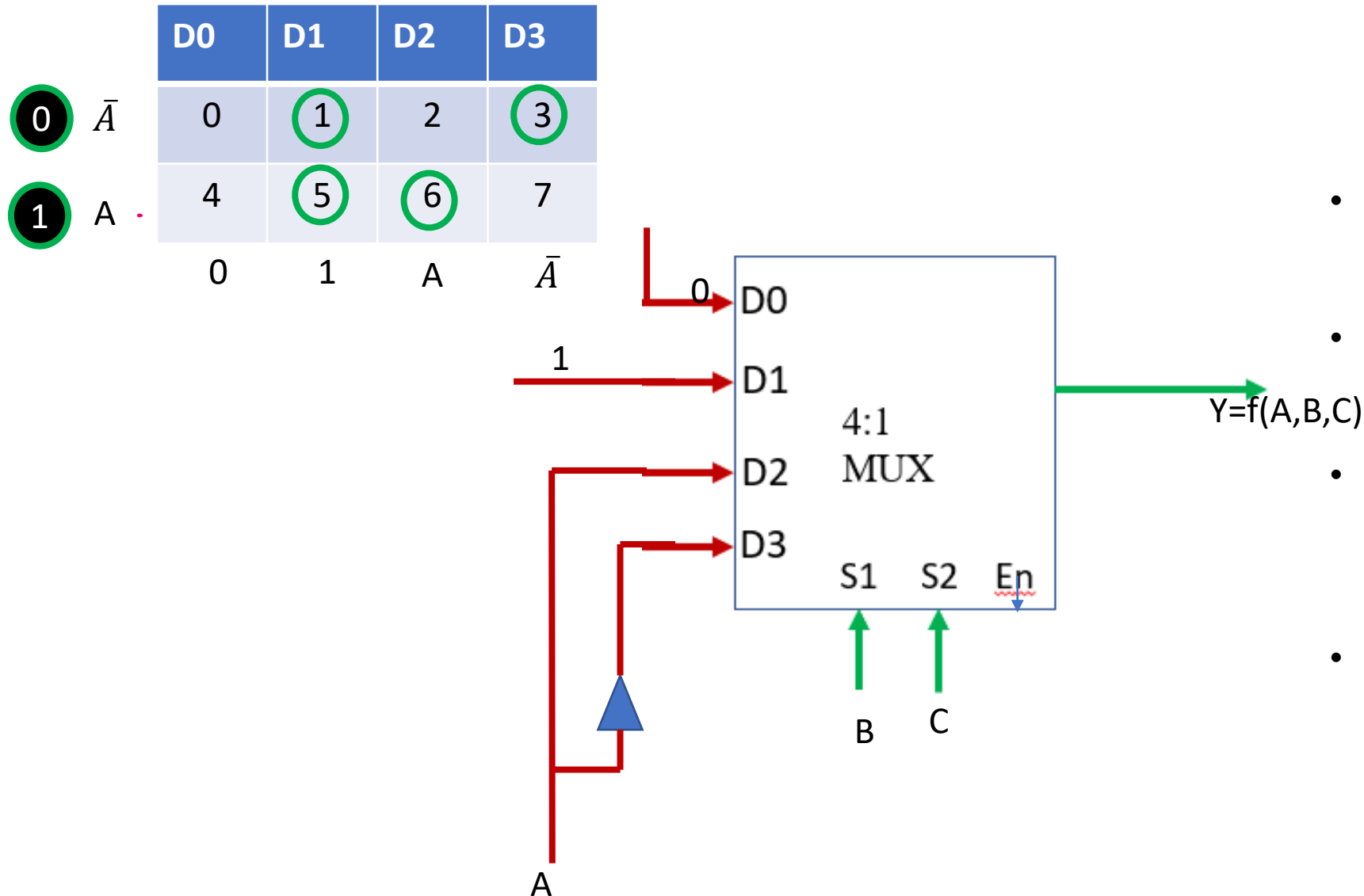- Implement the following Boolean function using 4:1 multiplexer  
 $f(A,B,C)=\sum(1,3,5,6)$ .




- In order to implement 8 input mux using 4:1 ,the 8 input mux function is first converted into 4 input mux (D0,D1,D2,D3) and two selection line ,one output.
- Two minterms in a column are not circled ,0 is applied to the corresponding input.
- Two minterms in a column are circled ,1 is applied to the corresponding input.
- If the minterms in the first row is circled,  $\bar{A}$  is applied to corresponding input
- If the minterms in the second row is circled, A is applied to corresponding input




- Implement the following Boolean function using 8:1 multiplexer  $f(A,B,C,D)=\sum(0,1,3,4,8,9,15)$ .

|             | D0 | D1 | D2 | D3        | D4        | D5 | D6 | D7 |
|-------------|----|----|----|-----------|-----------|----|----|----|
| 0 $\bar{A}$ | 0  | 1  | 2  | 3         | 4         | 5  | 6  | 7  |
| 1 $A$       | 8  | 9  | 10 | 11        | 12        | 13 | 14 | 15 |
|             | 1  | 1  | 0  | $\bar{A}$ | $\bar{A}$ | 0  | 0  | A  |

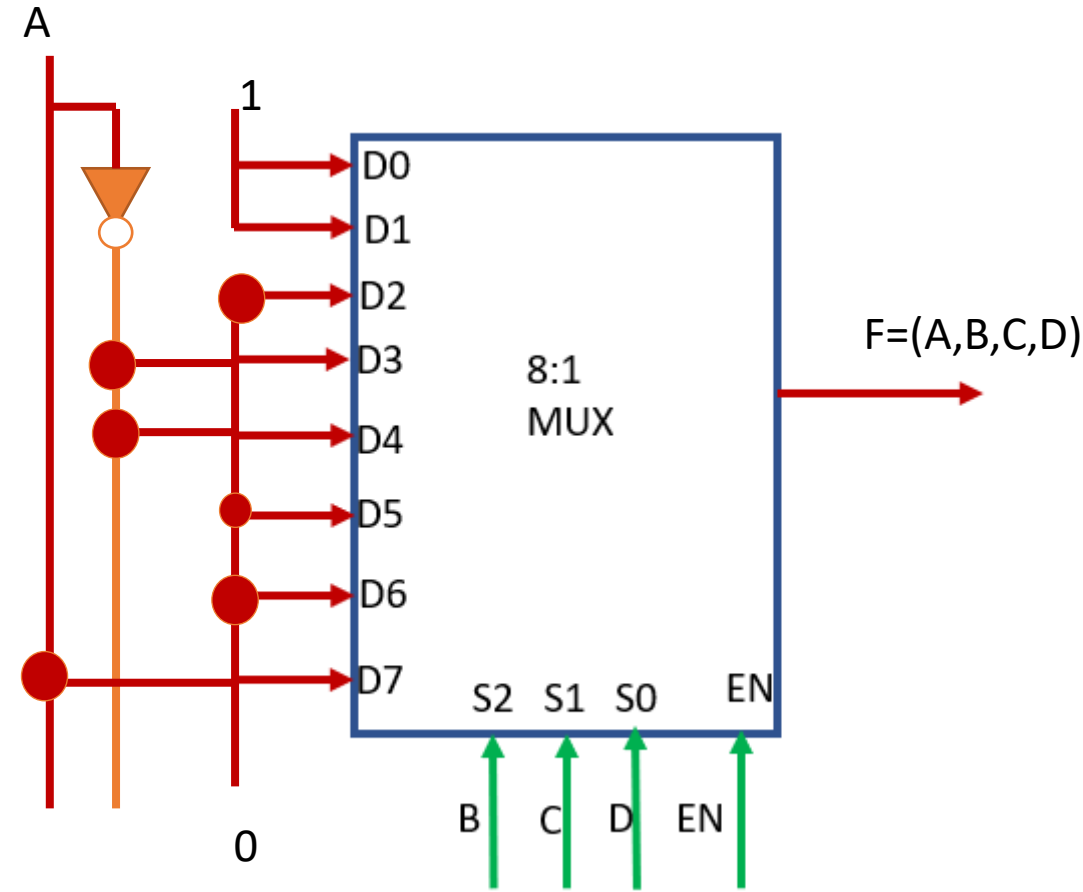

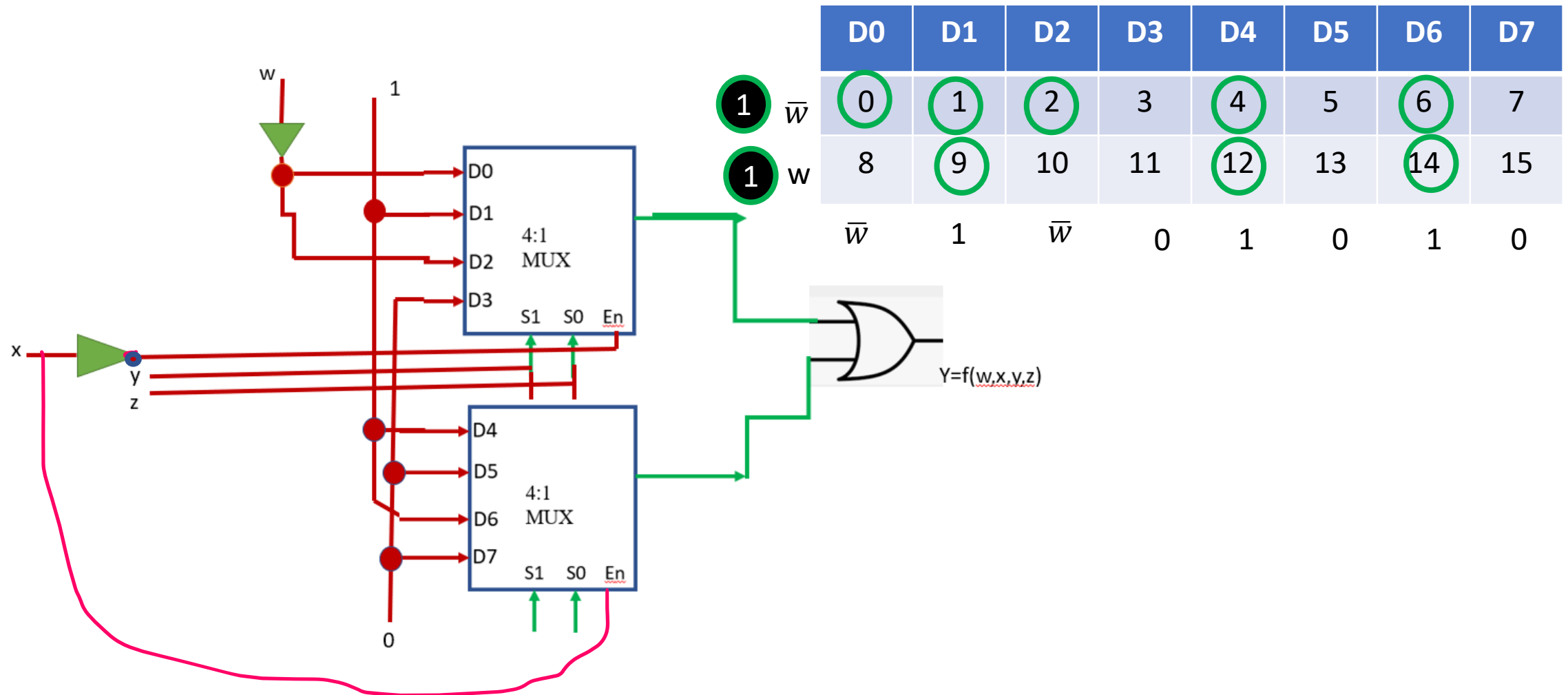- Implement the following Boolean function using 4:1 multiplexer  $f(w,x,y,z)=\sum(0,1,2,4,6,9,12,14)$ .



- Implement the following Boolean function using 8:1 multiplexer  $f(A,B,C,D)=\sum(0,2,6,10,11,12,13) + d(3,8,15)$

|   |           | D0        | D1 | D2 | D3 | D4 | D5 | D6        | D7 |
|---|-----------|-----------|----|----|----|----|----|-----------|----|
| 0 | $\bar{A}$ | 0         | 1  | 2  | 3  | 4  | 5  | 6         | 7  |
| 1 | A         | 8         | 9  | 10 | 11 | 12 | 13 | 14        | 15 |
|   |           | $\bar{A}$ | 0  | 1  | A  | A  | A  | $\bar{A}$ | 0  |

If we apply don't care 3 in the first table we get D3 as 1 .if we apply don't care 8 ,we get D0 as 1.But if we apply don't care 15 we get D7 as A. So the don't care we need to apply are (3,8)

|   |           | D0 | D1 | D2 | D3 | D4 | D5 | D6        | D7 |
|---|-----------|----|----|----|----|----|----|-----------|----|
| 0 | $\bar{A}$ | 0  | 1  | 2  | 3  | 4  | 5  | 6         | 7  |
| 1 | A         | 8  | 9  | 10 | 11 | 12 | 13 | 14        | 15 |
|   |           | 1  | 0  | 1  | 1  | A  | A  | $\bar{A}$ | 0  |

